

Class D audio amplifiers: theory and design

Revision A, June 2005, Sergio Sánchez Moreno, **coldamp** engineer

Introduction

A completely new technology for audio amplification has been evolving during the last 15-20 years that has a clear benefit over current widespread Class-A, and AB topologies. We are talking about the so-called "Class-D". This benefit is mainly its high power efficiency.

Fig. 1 shows typical efficiency curves vs. Output power for Class-B and Class-D designs:

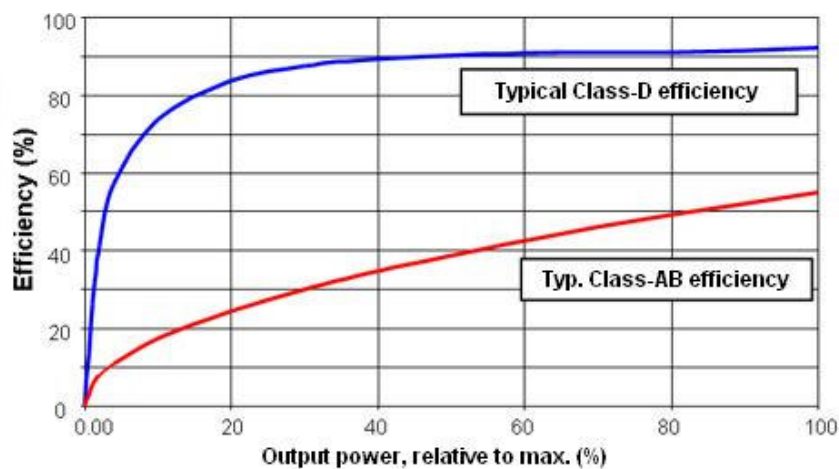


Figure 1 - comparison of typical practical efficiency for Class-D and Class-AB


The theoretically max. efficiency of Class-D designs is 100%, although over 90% is attainable in practice. Note that this efficiency is high from very moderate power levels up to clipping, and it is higher as the power increases (due to some fixed losses in the control and gate-drive circuitry). In Class-B, around 50% efficiency is achieved in practical use with music signals.

This high power efficiency translates into less power consumption for a given output power but, more important, it reduces heatsink requirements drastically. Anyone that has built or seen a high-powered audio amplifier has noticed that big aluminium extrusions needed to keep the electronics relatively cool. That devices account for an important part of the weight, cost and size of the equipment.

As we go deeper in the guts of this topology, we will notice that a well-behaving (low distortion, full range) Class-D amplifier requires to operate at quite high frequencies, in the 100KHz to 1MHz range, needing very high speed power and signal devices. This has historically relegated this class to uses where not full band is required and higher distortion levels are tolerable: that is, subwoofer use.

However, this has changed and thanks to today's faster switches, knowledge and the use of advanced feedback techniques it is possible to design very well performing Class-D amplifiers for the whole audio band featuring high power levels, small size and low distortion, comparable to that of good Class-AB designs. (From now on, I will refer to Class-A and AB topologies as "classical" ones).

Figure 2: Example of a 400W complete Class-D amplifier module

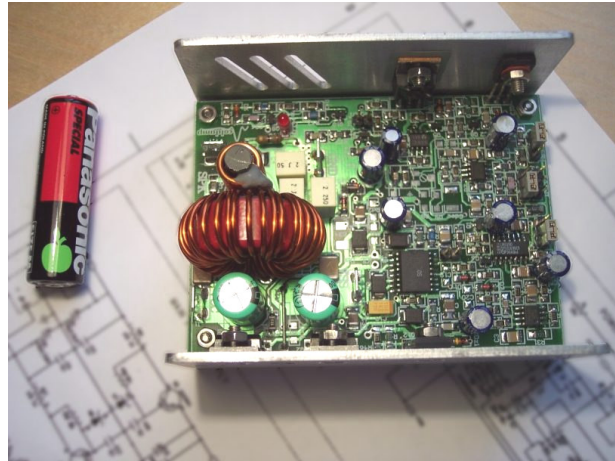

How it works

In classical amplifiers, at least one of the output devices (let them be bipolar transistors, mosfets or valves) is conducting at any given time. No problem so far, but they are also carrying a given current where there is a voltage drop between collector-emitter / drain-source or whatever applies. In definitive, as $P=V \cdot I$, they are dissipating power, even if there is no output a small quantity of current must pass through the transistors to avoid crossover distortion, so some dissipation is present. As the output voltage increases, for a given supply rails the voltage drop in the transistors will drop, but the current climbs. At saturation (clipping), VCE or VDS will be low, but current is quite high (V_{out}/R_{spk}). Conversely, at low power levels, current is small but voltage drop is large. This, in definitive, leads to a power dissipation curve that is not linear with output power and has a minimum, where maximum efficiency is reached (about 78% in pure Class-B designs, 25% in Class-A).

Class-D, on the other hand, bases its operation in switching output devices between 2 states, namely "on" and "off". Before entering into topologic details, we can say that in "on" state, a given amount of current flows through the device, while theoretically no voltage is present from drain to source (yes, almost every Class-D will use mosfets), hence power dissipation is 0. In the off state, voltage will be the total supply rails as it behaves like an open-circuit, but no current will flow (and that's very close to reality).

But how can our beloved audio signal be represented by an awful square wave with only two possible levels? Well, in fact it modulates some characteristics of this square wave so the information is there. Now we "only" have to understand the way the modulation is done and how to restore the amplified audio signal from it.

The most extended modulation technique used in Class-D is named "PWM" (Pulse Width Modulation": a square wave is produced that has a fixed frequency, BUT the time it is in "high" and "low" states is not always 50%, but it varies following the incoming signal: this way, when the input signal increases, the "high" state will be present more time than the "low" state, and the opposite when the signal is "low".

If we do some maths, the mean value of the signal in a single cycle is simply

$$V_{\text{mean}} = V_{\text{high}} * D + V_{\text{low}} * (1 - D), \text{ where } D = T_{\text{on}} / T, \text{ (duty cycle)}$$

T being the period of the signal, that is, $1 / f_{\text{sw}}$ (switching frequency).

For example, the mean value of a 50% duty cycle (both states are present the same amount of time) signal going from +50V to -50V is: $50 * 0.5 + (-50) * 0.5 = 0V$. In fact, the idle (no signal) output of a Class-D amplifier is a 50% duty cycle square signal switching from the positive to the negative rail.

If we modulate the input up to the maximum, we will have a near-100% duty-cycle. Let's put 99%: $V_{\text{mean}} = 50 * 0.99 + (-50) * 0.01 = 49V$.

Conversely, if the signal is lowest, we need near-0% (lets use 1%), so $V_{\text{mean}} = -49V$.

PWM is usually generated by comparing the input signal with a triangle waveform as shown in the figure at fig.3. The triangle wave defines both the input amplitude for full modulation and the switching frequency

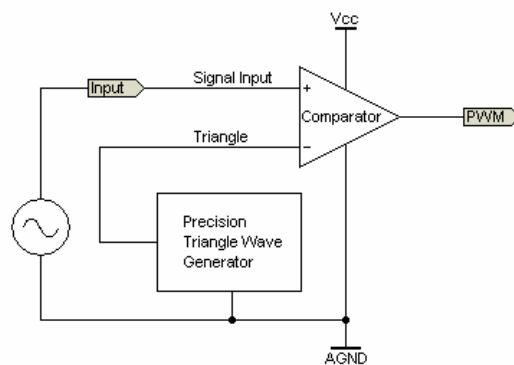


Figure 3 - Basic method for PWM generation using a triangle wave.

Fig. 4 shows a typical PWM signal modulated by a sine wave. Notice that it is designed so signals between -1 and 1V will produce 0% to 100% duty cycles, 50% corresponding to 0V input.

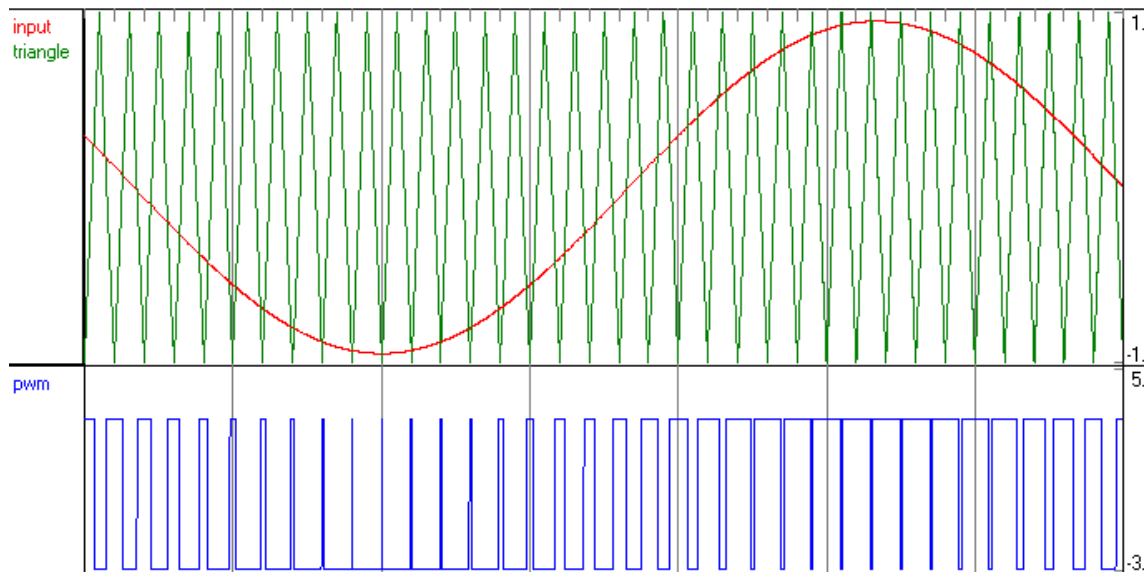


Figure 4 - Aspect of a PWM modulated signal

Note that, for a correct representation of the signal, the frequency of the PWM waveform will be needed to be much higher than that of the maximum input frequency. Following Nyquist theorem, we need at least twice that frequency, but low distortion designs use higher factors (typically 5 to 50).

The PWM signal must then be drive a power conversion circuitry so that a high-power PWM signal is produced, switching from the (+) to (-) supply rails (assuming a half-bridge topology).

The spectrum of a PWM signal has a low freq. component that is a copy of the input signal's spectrum, but also components at the switching frequency and harmonics of it that should be removed in order to reconstruct the original modulating signal. A power low-pass filter is then, necessary. Usually, a passive LC filter is used, because it is (almost) lossless so no dissipation is theoretically produced on it.

Its cutoff frequency must be somewhat greater than our highest audio frequency of interest so it doesn't attenuate it, but at the same time we want it to have a rejection at the switching frequency and above as high as possible. A basic 2nd order LC filter has a -40dB/decade rolloff so it can provide good attenuation at the switching frequency if it is high enough. As will be seen later, the response of a LC filter is dependent on the load, in fact it is part of the filter. This is one of the problems to solve in Class-D designs. Again, only a handful of good Class-D amplifiers use feedback techniques that include the output filter to compensate that variations and have a nearly load independent frequency response, as well as to reduce distortion produced by nonlinearities in the filter.

Well designed Class-D amplifiers have a higher order filter and/or special carrier suppression sections in order to avoid problems with EMI.

Topologies:

Class-D topologies are basically two: half-bridge (2 output devices are used) and full-bridge (4 output devices). Each one has its own advantages. For example, half-bridge is obviously simpler and has more flexibility as a half-bridge amplifier can be bridged as with classical topologies. If it is not correctly designed and driven, can suffer from “bus pumping” phenomena (transfer current to the power supply that can make it increase its voltage producing situations dangerous to the amplifier, supply and speaker).

Full bridge requires output devices rated for half the voltage as an half-bridge amplifier of the same power, but it is more complicated.

Figs. 5a and 5b show both topologies conceptually. Obviously, a lot of componets like decoupling capacitors, etc are missing.

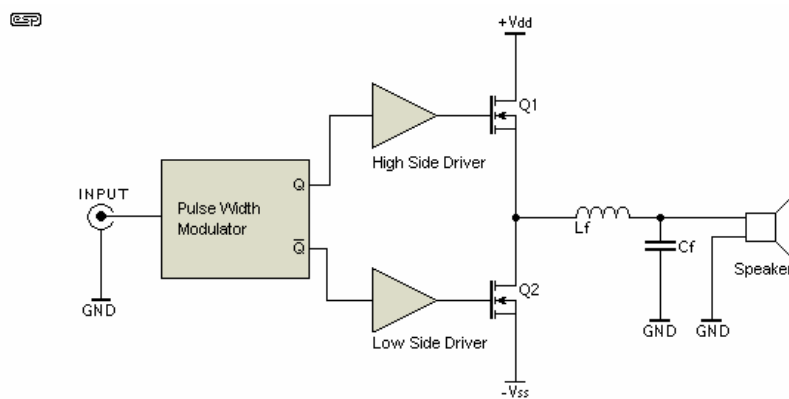


Figure 5a - Half bridge Class-D topology

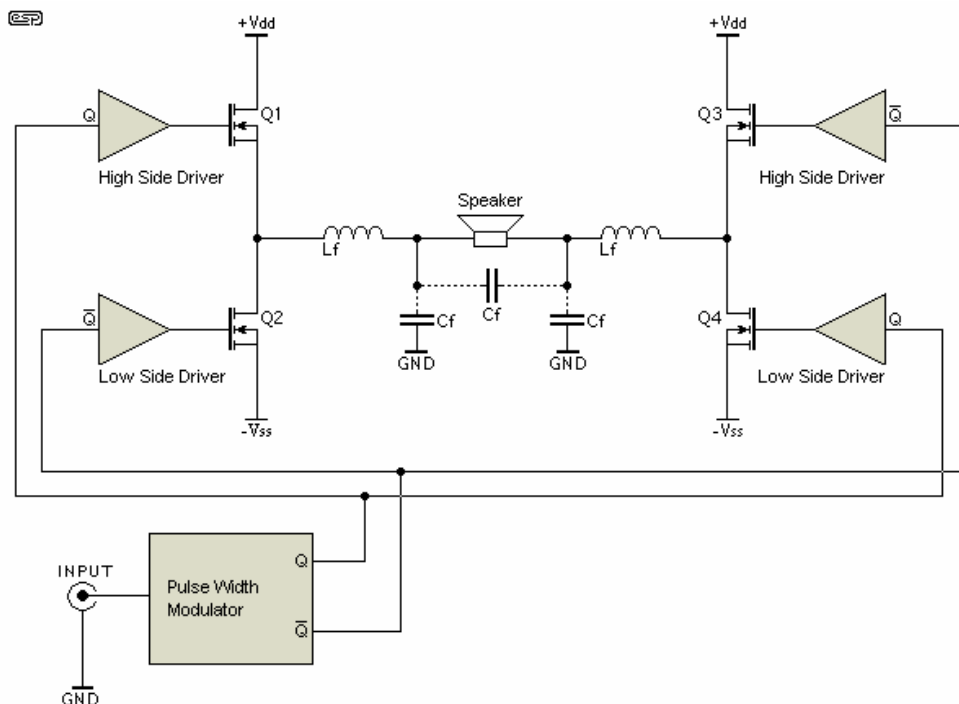


Figure 5b - Full bridge Class-D topology

Note that the, opposing to half-bridge, full bridge uses only one supply rail (not bipolar). Hence, in each speaker lead, $\frac{1}{2}$ of V_{cc} voltage is present. As it is connected differentially, it doesn't see any DC if everything is well balanced.

The filter may be implemented by means of a single capacitor across the loudspeaker, by a pair of caps to ground, or in some cases by both (as shown by the dotted lines connecting the caps).

For the rest of the document, we will concentrate on half-bridge topologies, although the vast majority of the ideas are also applicable to full-bridge designs.

Half bridge design

The operation of the half bridge circuit depicted in fig. 5a is as follows: When Q1 is on (corresponding to the positive part of the PWM cycle), the switching node (inductor input) is connected to V_{cc} , and current starts to increase through it. The body diode of Q2 is reverse biased. When Q2 is on (negative part of the PWM cycle), the body diode of Q1 is reverse biased and the current through L_f starts to decrease. The current waveform in L_f is triangular shaped.

Obviously, only one of the transistors must be on at any time. If for any reason both devices are enhanced simultaneously, an effective short-circuit between the rails will be produced, leading to a huge current and the destruction of the mosfets. To prevent this, some "dead-time" (a small period where both mosfets are off) has to be introduced.

L_f in conjunction with C_f and the speaker itself form the lowpass filter that reconstructs the audio signal by averaging the switching node voltage.

Timing is critical in all this process: any error as delays or rise-time of the mosfets will ultimately affect efficiency and audio quality. So all the involved components must be high-speed. Dead-time also affects, so it must be minimized but at the same time have a value enough to ensure that under no circumstance both mosfets are on at the same time. Typical values are 5 to 100ns.

Gate driving

To ensure fast rise/fall times of the mosfets, the gate driver must provide quite a high current to charge the gate capacitance during the switching interval. Typical 20-50ns rise/fall times are needed, requiring more than 1A of gate current.

Note that the figure schematic uses both N-channel mosfets, because, although some designs use N and P channel complementary devices, that is, IMHO, suboptimal due to the difficulty of obtaining suitable P devices and matched pairs. So let's concentrate on N-channel only half-bridges.

Note that, in order to drive a mosfet on, a voltage above V_{th} must be present between its gate and source. The lower mosfet has its source connected to $-V_{ss}$, so its drive circuit has to be referred to that node instead of GND.

However, the upper mosfet is more difficult to drive, as its source is continuously floating between $+V_{cc}$ and $-V_{cc}$ (minus drops due to on-resistance). However, its driver must be also floating on the switching node and, what's more, for the on-state, its voltage must be several volts above $+V_{cc}$ so a positive V_{gs} voltage is created when Q1 is on. This also implies a voltage shifting so the modulator circuit can communicate correctly with the driver.

This is one of the major difficulties of Class-D design: gate drive. To solve the issue, several approaches are taken:

- Transformer gate drive: useful in half-bridge power supplies where duty-cycle doesn't vary widely. In audio amplifiers, however, it can go from 0% to 100%, so a problem exists as the signal is AC coupled and some form of DC restoration would be needed.
- Discrete gate driving: some designs use transistors to perform both the level shifting and the mosfet drive. But there is a problem: we need a voltage that is higher than $+V_{cc}$.
- Integrated drivers: there are a number of mosfet drivers in the market, optimized for high speed, that can be used. Again, a voltage higher than V_{cc} is needed as well as level shifting.

Fig.6 depicts some possibilities for gate driving

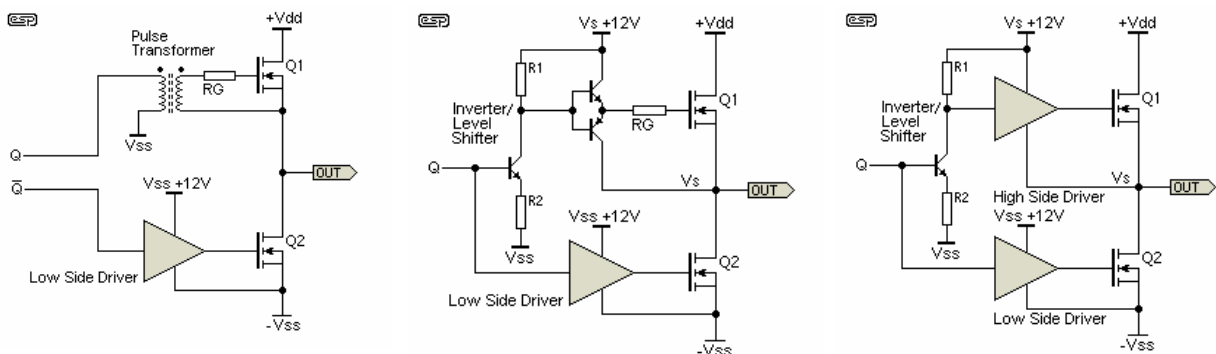


Figure 6a - Transformer coupled high side driver

Figure 6b - BJT high side driver with level shifting

Figure 6c - IC high side driver with level shifting

Note that circuits in figures 6b and 6c have their PWM input referred to $-V_{ss}$ so may require previous level shifting of the comparator output, that will normally be referred to GND. Fig 6a will require level shifting of the inverted PWM only, as the transformer input can be referenced to GND as in the picture.

We have still one problem to solve: obtaining 12V above V_S (the switching node). We can add another power supply, isolated from the main one, which (-) is connected to V_S . This solution can be impractical, so other techniques are commonly used. The most widespread is "bootstrap".

Bootstrap technique uses a charge pump built with a high speed diode and a capacitor. The switching produces the pulses needed to charge the capacitor:

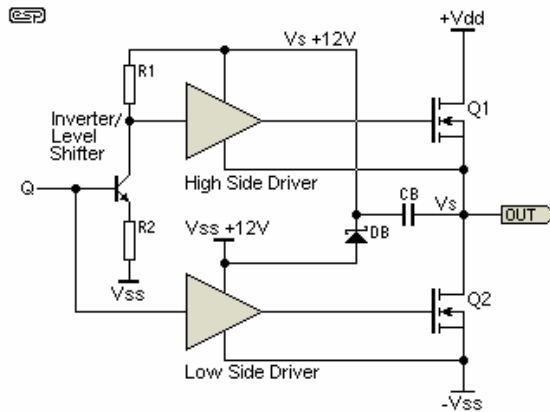


Figure 7 - Bootstrap capacitor provides the high side driver supply voltage

This way, the only auxiliary power supply needed is 12V referenced to $-V_{ss}$ that is used for powering both the low side driver and the charge pump for the high side driver. As the average current from this supply is low (although there are high current charging peaks during the switching events, they last only 20-50ns, twice during a cycle, so the average is quite low, in the 50-80mA range), this supply is easily obtained from the negative rail with a simple 12V regulator (paying attention to its maximum input voltage rating, of course).

As can be seen, implementing all the functions needed for proper mosfet driving in a half bridge is not easy. Several manufacturers have developed chips designed solely for this purpose. They accept TTL inputs and perform all the necessary functions (level shifting, generation of bootstrap voltage, some even dead time, and gate driver buffer) in a single chip, with very accurate and fast timing. Examples of this are IR21XX series from International rectifier or LM51XX series from National Semiconductor. Some of them offer even an useful shutdown pin.

Level shifting

As can be seen from the previous figures, in order to excite the mosfet driver, the PWM signal has to be referred to $-V_{ss}$. So, as the modulator usually works from +/-5 to +/-12V, typically, a level shifting function is needed. One can choose to shift the level of the PWM signal and then generate the inverted version, or generate both outputs and invert both of them. It depends, for example, on the comparator type used (if complementary outputs are available, the decision is made).

Level shift can be performed with a single or two-transistor circuit, similar to the one depicted in fig. 6 before the high side driver.

In any case, it is important to simulate the behaviour of the comparator and level shifter, as they can introduce considerable delays and timing errors if not properly designed.

Output filter design

The output filter is one of the most important parts of the circuit, as the overall efficiency, reliability and audio performance depends on it. As previously stated,

a LC filter is the common approach, as it is (theoretically) lossless and has a -40dB/decade slope, allowing for a reasonable rejection of the carrier if the parameters of the filter and the switching frequency itself are properly designed.

The first thing to do is to design the transfer function for the filter. Usually, a Butterworth or similar frequency response is chosen, with a cutoff frequency slightly above the audio band (30-60KHz). Have in mind that one of the design parameters is the termination load, that is, the speaker impedance. Usually, a typical 4 or 8 ohm resistor is assumed, but that would produce variations in the measured frequency response in presence of different speakers. That must be compensated for by means of proper feedback network design. Some manufacturers simply leave it that way so the response is strongly dependent on the load. Surely a non-desirable thing.

The design can be done mathematically or simply use one of the many software programs available that aid in the design of LC filters. After that, a simulation is always useful. Figure 8 shows a typical LC filter for Class-D amplifiers and its typical frequency response.

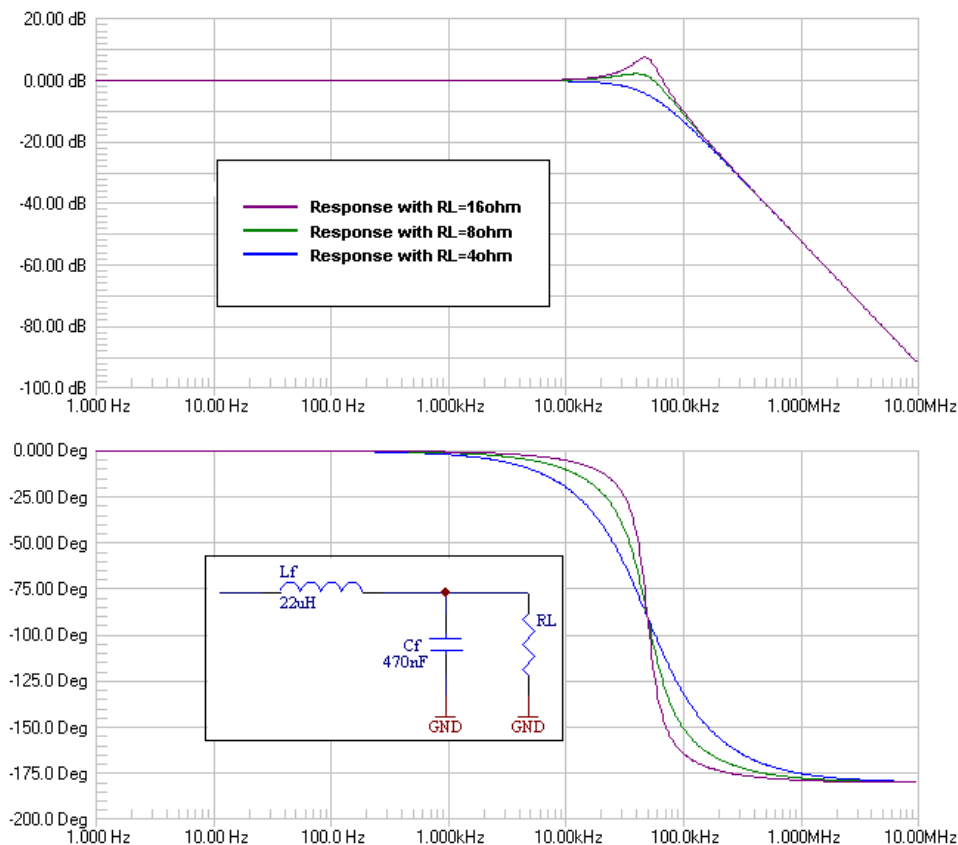


Figure8 - frequency response of a typical Class-D LC 2nd order filter with several loads.

This simple filter has a -3dB cutoff frequency of 39KHz (with 4 ohm load), and suppresses the carrier as much as 31dB at 300KHz. For example, if our supply rails are $\pm 50\text{V}$ (enough for about 275W at 4 ohms), the residual ripple will have an amplitude of about 1Vrms.

This ripple is, obviously inaudible, and 1Vrms will dissipate only around 200mW in a typical tweeter (not likely a problem). However, care must be taken as the

speaker wires can become an antenna and affect other equipment. In fact, although a couple of volts rms of ripple can seem low enough to run your speakers safely, EMI can be a concern, so the less carrier level you have, the better. For further rejection, higher order filters are used (with the potential disadvantage of increased phase shift in the audio band), although there are other clever ways to do it, as very selective bandstop or "notch" filters tuned to the carrier frequency (if it is fixed, and that only happens in synchronous designs as the one described).

Now with the components...

The output inductor has to withstand the whole load current, and also have storage capability, as in any non-isolated switching converter (Class-D half bridge design is in fact analogous to a buck converter, its reference voltage being the audio signal).

The ideal inductor (in terms of linearity) is an open-core one, but the size and number of turns required for typical Class-D operation usually makes it impractical, so a core is normally used in order to reduce turns count and also provide a confined magnetic field that reduces radiated EMI. Powder cores are the common choice, or equivalent materials. It can also be done with ferrite cores, but they must have a "gap" where energy is stored.

Wire size must also be carefully chosen so DC losses are low (requiring thick wire) but also skin effect is reduced (AC resistance must also be low).

Many core manufacturers such as Micrometals or Magnetics offer their own software, very useful to design the output inductor as they help choosing the right core, wire size and geometrical parameters.

Inductor core shape can be a drum core, gapped ferrite RM core, or toroidal powder core, among others. Drum cores have the problem that their magnetic field is not enclosed, hence producing more radiated EMI. RM cores solve this problem but have most of the coil enclosed, so cooling problems may arise as no airflow is possible. IMHO, toroids are preferred because they feature both closed magnetic field that helps control radiated EMI, a physically open structure that allows proper cooling, and easy and economical winding, as they don't need bobbins.

Figure 9 shows different types of cores:



Figure 9a - Toroid core

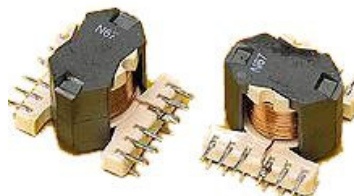


Figure 9b - RM core



Figure 9c - Drum core

The capacitor usually falls in the 200nF to 1uF range, has to be of good quality too, in order to ensure good high frequency behaviour and low losses and of course has to be rated for the whole output voltage. Usually, polypropylene capacitors are chosen. Not to say, don't use electrolytics!

Feedback

As I have stated previously, timing errors can lead to increased distortion and noise. This cannot be skipped and the more precise it is kept, the better the design will perform.

Anyway, open loop Class-D amplifiers are not likely to satisfy demanding specifications, so (negative) feedback is almost mandatory.

There are several approaches: the most simple and common is to take a fraction of the switching signal, promediate it by means of a passive RC low pass filter and feed it back to the "error amplifier".

To put it simple, the error amplifier is an opamp placed in the signal path (before the PWM comparator) that sums the input signal with the feedback signal to generate a error signal that the amps automatically minimizes (this is the concept of every negative-feedback system, anyway).

ESP

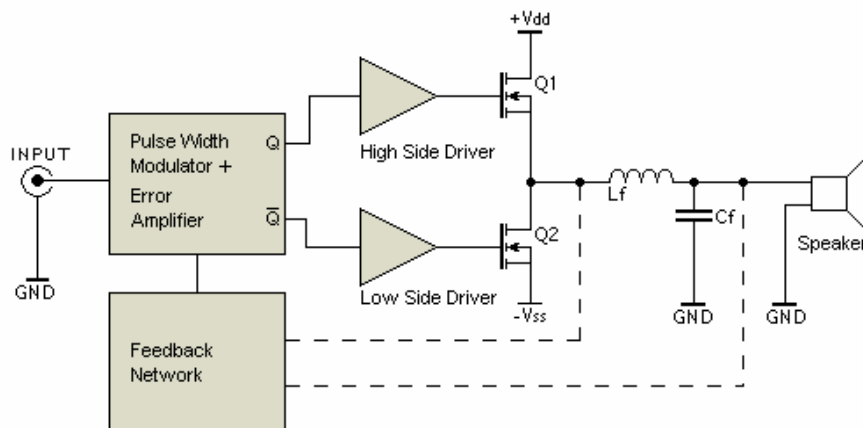


Figure 10 - Typical Feedback Network Connections

Although good results are obtained this way, there is still a problem: load dependency, due to the speaker being an integral part of the filter, hence affecting its frequency response as shown above.

Some more advanced amplifiers take the feedback signal from the very output, trying to compensate this. This way, a constant frequency response is obtained, with the further gain that the inductor resistance contributes much less to the output impedance, so it is kept lower, hence damping factor is higher (higher speaker control).

But taking feedback after the filter is not an easy task: the LC introduces a pole and hence a phase shift that, if not properly compensated, will make the amp become unstable and, ultimately, oscillate. Feedback may be taken from both the

switching node and the filter output. Although this can give very good results, it is still difficult to maintain stability because of the phase shift through the output filter.

Other topologies

Pure PWM (based on triangle generators, also called 'natural sampling PWM') is not the only way to go in order to construct a Class-D amplifiers. Some other topologies have arisen, many of them based on auto-oscillation, where the hysteresis in the comparator and delays between the comparator and power stage can be taken into account to design a system that oscillates by itself in a somewhat controllable manner.

Although simpler, these designs have some disadvantages, IMHO. For example, the switching frequency is not fixed, but depends on the signal amplitude. This makes output notch filters ineffective, yielding higher ripple levels. Besides, when several channels are put together, the difference in switching frequency between them can produce audible beat tones that can become very annoying. This can also happen of course with synchronous design as the one described here, but there is a simple solution - use the same clock for all the channels.

Self oscillating designs in particular have some other difficulties like start-up: special circuitry may be needed that forces the amplifier to start oscillating. Conversely, if for any reason the oscillation stops, you could end up with an 'always-on' MOSFET, and thus a large amount of DC at the output, followed almost immediately by a dead loudspeaker. Of course, these issues can be solved with proper design, but the added complexity can void the initial simplicity, thus no gain is obtained.

Low distortion in a PWM amplifier requires a very linear triangle waveform, along with a very fast and accurate comparator. At the high operating frequencies needed for optimum overall performance, the opamps used need to have a wide bandwidth, extremely high slew rate, and excellent linearity. This is expensive to achieve, requiring premium devices. Some of these constraints are relieved somewhat by self oscillating designs (therefore making them slightly cheaper), but this is not an effective trade-off for the most part.

Clocked designs (fixed frequency) are not easier to make than self-oscillating or modulated switching frequency designs, but are certainly far more predictable and tend to have fewer problems overall. The ability to synchronise multiple amplifiers ensures that mutual interference is minimised. An 'advantage' claimed by the proponents of non-clocked and 'random switching' designs is that the RF energy on the speaker leads is spread over a wide frequency range, potentially making such amplifiers more likely (or perhaps less unlikely) to pass EMI testing. From an overall perspective, this is more likely to be a hinderance than a benefit, as it is no longer possible to optimise the filter network for maximum switching frequency rejection.

There are also PWM amps that claim to be truly 'digital', using One-Bit™ technology, or generating the PWM signal directly from the PCM data stream.

Although the manufacturers of such amplifiers will naturally proclaim their superiority over all others, such self-praise should generally be ignored. Implementing feedback in a 'pure' digital design is at best difficult, and may be impossible without using a DSP (digital signal processor) or resorting to an outboard analogue feedback system. Including additional ADCs and DACs (analogue to digital converters and vice versa) is unlikely to allow the amplifier to be any 'better' than the direct analogue methods described in this article.

A relative newcomer to the scene is the Sigma-Delta modulator, however at the time of writing this still has problems (challenges in corporate speak). The main issue is that the transition rate is too high, and it must be reduced to accommodate real-world components - particularly the power switching MOSFETs.

The 'pure' digital solutions described above have another shortfall, and that's the fact that the number of different pulse widths is finite, and determined by the clock speed. A digital system can only switch on a clock transition. Based on currently available information, only around 8 x oversampling is possible if a digital noise shaping filter is added to the system. An analogue modulation system has an effectively infinite number of different pulse widths, but this is not possible with any true digital implementation.

These latter comments cover a very complex area, one is outside the scope of this article. However, even the scant information above will give most readers far more information that is commonly available - especially from manufacturers of digital Class-D amplifiers.

Some final notes...

As a conclusion, Class-D amplifiers have evolved a lot since they were first invented, achieving levels of performance similar to conventional amplifiers, and even better in some aspects, like an inherent low output impedance that allows effortless bass. All this, with the great advantage of high efficiency. Of course, only if they are properly designed.

However, although very attractive, Class-D designs are not very DIY friendly. In order to achieve a properly working design in terms of efficiency, performance and EMI, very careful PCB layout is mandatory, some component selections are critical and of course proper instrumentation is absolutely required.

This article has been written in order to throw some light about the internals, advantages and difficulties of this not very well-known (and even less well understood) technology. Everyone thinks that "Class-D" stands for "Digital". I hope that after reading this article, no-one thinks that any more.

The author wants to express his acknowledge to:

Rod Elliot, for his unvaluable help at the time of writing and editing this document, his appropriated additions and his willingness to publish it on his webpage, *The Audio Pages* (www.sound.au.com)